

1231**Code : 15EE34T**Register
Number

--	--	--	--	--	--	--

III Semester Diploma Examination, Nov./Dec. 2017**DIGITAL ELECTRONICS****Time : 3 Hours]****[Max. Marks : 100**

- Note :** (i) Answer any **six** questions from Part – A. Each question carries **5** marks.
(ii) Answer any **seven** questions from Part – B. Each question carries **10** marks.

PART – A

1. Define IC and list the advantages of IC over discrete components. **5**
2. Explain ASCII and gray codes. **5**
3. Write rules of Boolean algebra. **5**
4. Explain OR & NAND gates with logic diagram, Boolean function and truth table. **5**
5. Define multiplexer. List its applications. **5**
6. Explain Half adder with block diagram, truth table and logic diagram using AND & XOR gates. **5**
7. Explain the operation of 4 bit SISO shift register. **5**
8. Explain the working of JK flip-flop using NAND gates. **5**
9. Explain CMOS interfacing with switch and LED. **5**

PART – B

10. (a) List the advantages and disadvantages of CMOS. **5**
- (b) (i) Add $(78)_{10}$ and $(98)_{10}$ in Binary. **3**
- (ii) $(AC6)_{16}$ & $(B59)_{16}$ **2**

[1 of 2]**[Turn over**

11. (a) Perform binary subtraction using 2's complement and justify the answer. **6**
(i) $(0100)_2$ from $(1010)_2$
(ii) $(111001)_2$ from $(100011)_2$
(b) Convert the following binary numbers into decimal equivalent. **4**
(i) 10101.101_2
(ii) 10110101_2
12. (a) Define parity bit and mention its importance. **5**
(b) State De-Morgan's theorem with equations. **5**
13. (a) Simplify Boolean expression using K-map and draw the logic diagram.
 $F = \bar{A} \bar{B} \bar{C} + \bar{A} B \bar{C} + A B C + A \bar{B} C$ **6**
(b) Explain the commutative and associative laws of Boolean algebra. **4**
14. (a) Explain the working of 10 line to 4 line priority encoder 74147. **8**
(b) Define combinational logic circuit. **2**
15. (a) Explain the working of 1 : 4 DEMUX with block diagram, truth table and logic diagram. **5**
(b) Explain seven segment display with a diagram. **5**
16. (a) Explain the working of clocked RS flip-flop using NAND gates. Write the truth table. **6**
(b) Define level and edge triggering. **4**
17. (a) Explain the working of 4 bit binary asynchronous counter using JK flip-flops with block diagram, truth table and timing diagram. **8**
(b) List the applications of counters. **2**
18. (a) Explain the working of 3 bit synchronous up counter. **6**
(b) Define DAC & list the types. **4**
19. (a) Explain the operation of successive approximation ADC with block diagram. **7**
(b) List the types of memories. **3**