

Register
Number

--	--	--	--	--	--	--	--	--	--

III Semester Diploma Examination, April/May-2019

DIGITAL ELECTRONICS

Time : 3 Hours]

[Max. Marks : 100

- Instruction :** (i) Answer any **six** questions from PART – A. Each question carries **5** marks.
(ii) Answer any **seven** questions from PART – B. Each question carries **10** marks.

Published By:

PART – A

1. Define : 5
 - (i) Fan-out
 - (ii) Propagation delay
 - (iii) Operating temperature
 - (iv) Power dissipation
 - (v) Positive logic
2. (i) List the various number systems with their radix. 4
(ii) Define bit and byte. 1
3. List the characteristics of TTL logic family. 5
4. Define Multiplexer. List applications of it. 5
5. What is logic gate ? Write symbol and truth table of AND & XOR gates. 5
6. Explain half adder with truth table. 5
7. Draw the RS flip-flop logic diagram using NAND gates with truth table. 5
8. Define shift register. Mention the applications of shift registers. 5
9. What is interfacing ? Explain interfacing of TTL with switch. 5

PART - B

10. (a) Define parity bit and explain its importance. 4
 (b) Add the following : 6
 (i) $78_{10} + 98_{(10)} = ? \text{ BCD}$
 (ii) $1101.101_{(2)} + 111.011_{(2)} = ?$
 (iii) $6E_{(16)} + C5_{(16)} = ?$
11. Find the value of 'X' in the following : 10
 (i) $93_{(10)} = X_{(2)}$
 (ii) $498_{(10)} = X_{(16)}$
 (iii) $110.0110_{(2)} = X_{(10)}$
 (iv) $B2F8_{(16)} = X_{(10)}$
 (v) $AC.6_{(16)} = X_{(2)}$
12. (a) Realize the NAND gate as NOT, AND & OR gate. 5
 (b) State Demorgan's theorem with equations. 5
13. (a) What is K-map ? Define POS and SOP terms. 6
 (b) Simplify Boolean expression : 4

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC + A\bar{B}C$$
14. (a) Define Demultiplexer. Explain operation of 1 : 4 demultiplexer. 5
 (b) Explain the working of 10 line - 4 line 74147 IC with pin diagram and truth table. 5
15. (a) Define Encoder and Decoder. 4
 (b) List and explain the types of seven segment display with working. 6
16. (a) Explain the working of 4-bit binary synchronous counter using JK flip-flop with block diagram, truth table and timing diagram. 8
 (b) Define flip-flop. 2
17. (a) Explain the operation of SISO shift register with truth table and block diagram. 6
 (b) List the applications of flip-flops. 4
18. (a) Explain the operation of binary weighted register type DAC. 5
 (b) Define Memory. List the types. 5
19. (a) Explain the working of JK flip-flop using NAND gates with truth table. 6
 (b) Explain interfacing of CMOS with relay. 4